
 
 
 


# Xetroc 1.0



F.B.

# From 0 and 1 to CPU

# Inverter & NAND Gate

 


# 1-Bit Adder

 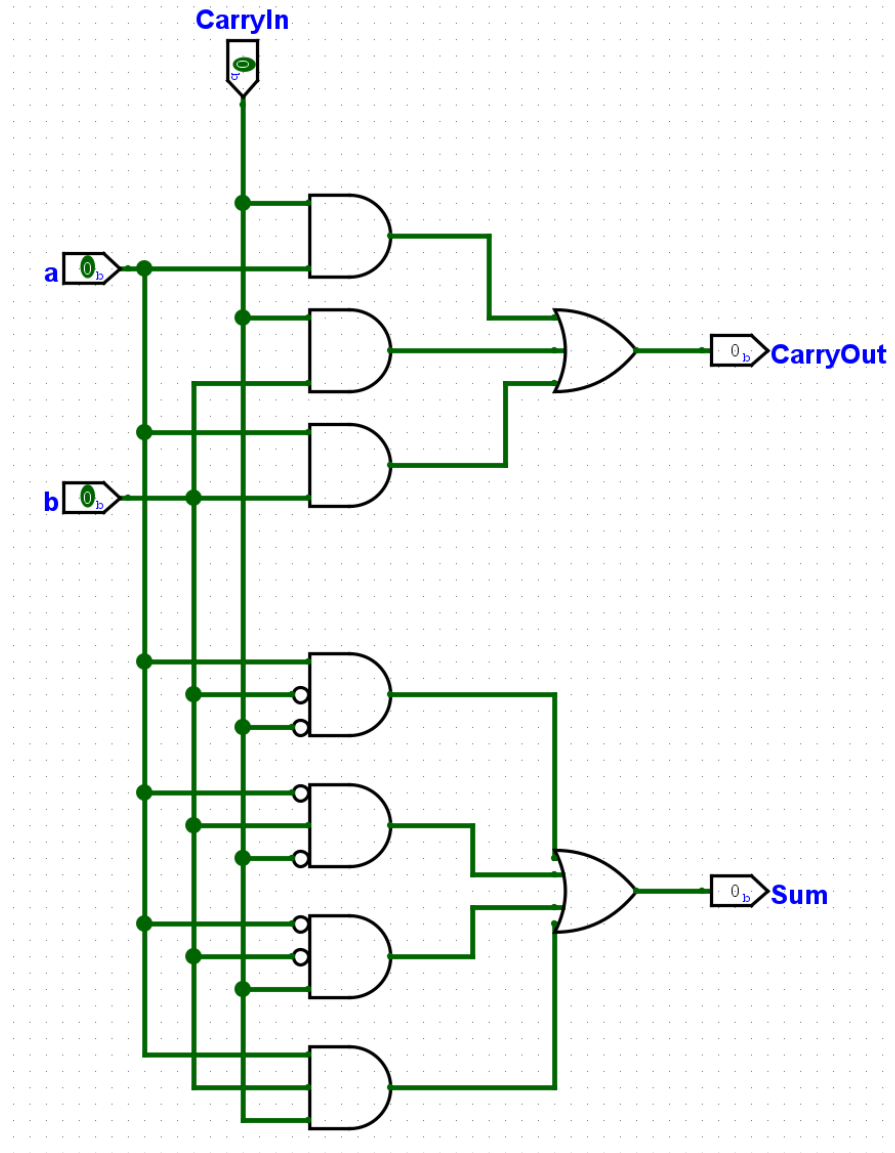



CarryIn	a	b	CarryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# 32-Bit Adder (Carry Ripple Adder)

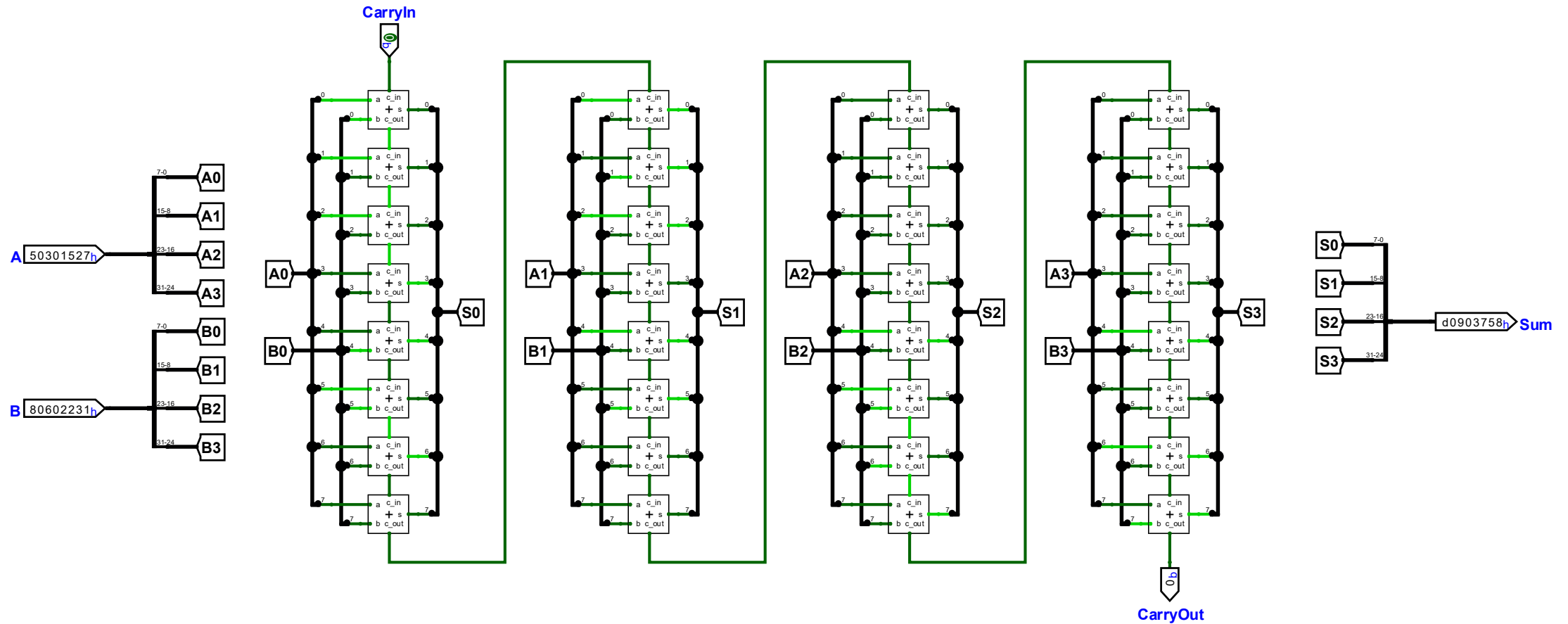

# ALU


ALUControl				
0	0	0		B
0	0	1		-B
0	1	0		0
0	1	1		A
1	0	0		A + B
1	0	1		A - B
1	1	0		A & B
1	1	1		A   B

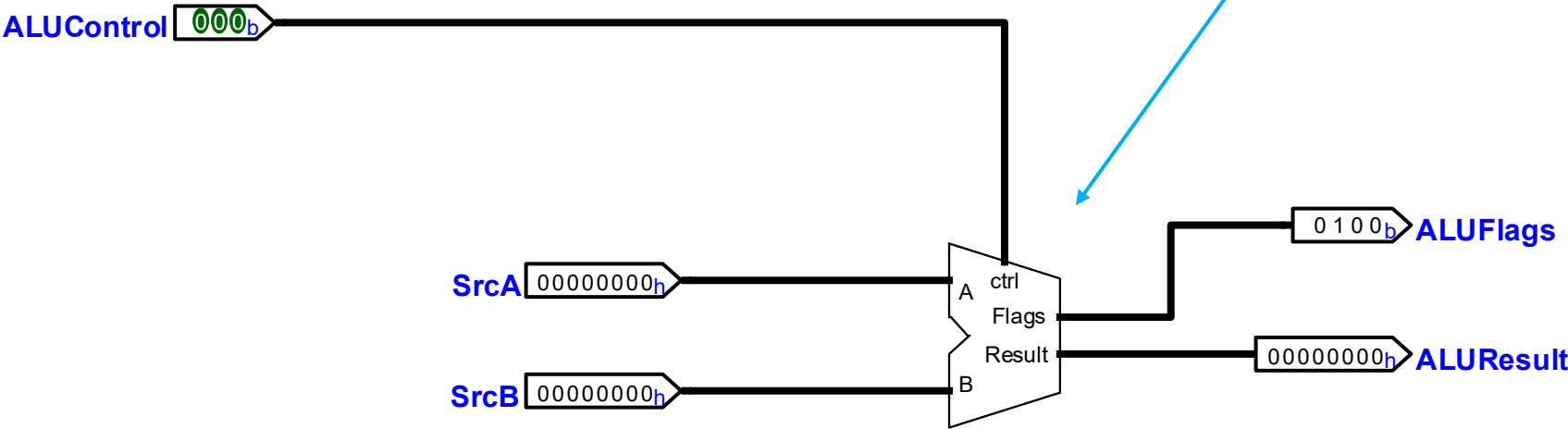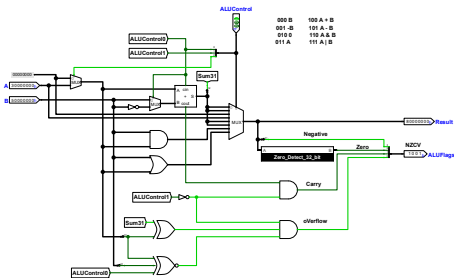


# ALU with Accumulator

D-Flipflop (MS)  
(used for all registers)

D	WE	R	CLK	Q'	
0	0	0	x	Q	no change
1	0	0	x	Q	no change
x	x	1	x	0	static reset
0	1	0	↑	0	edge triggered write
1	1	0	↑	1	edge triggered write

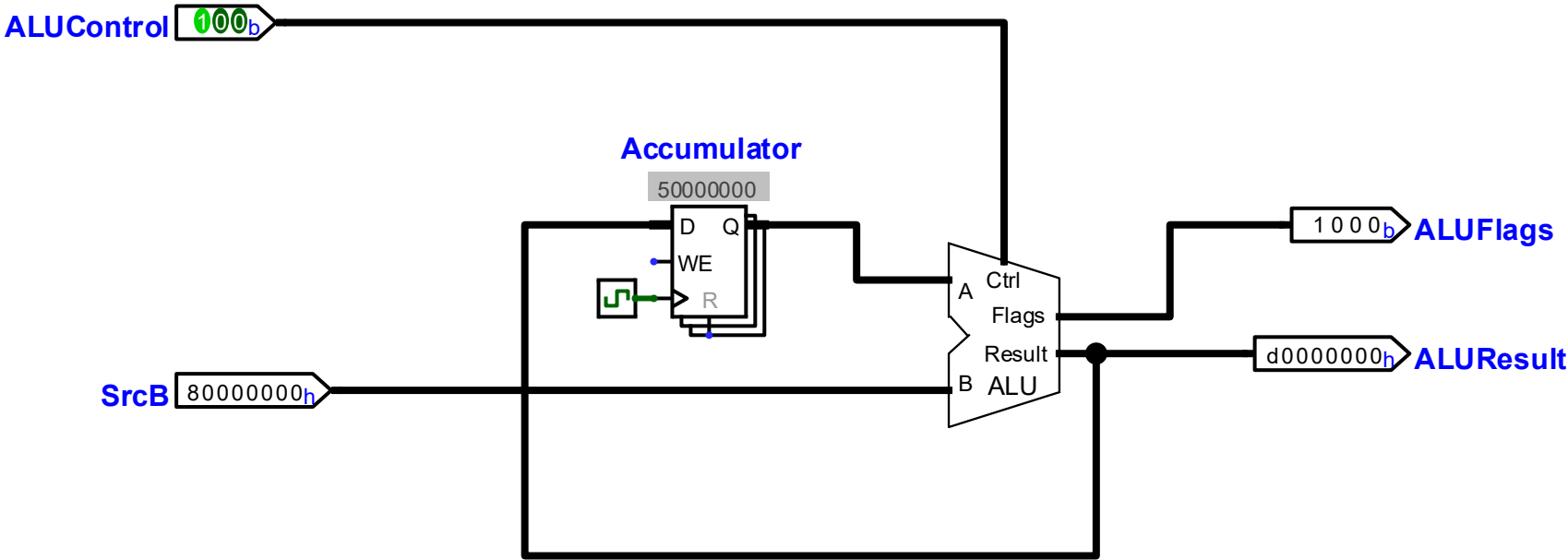

# ALU with Register File

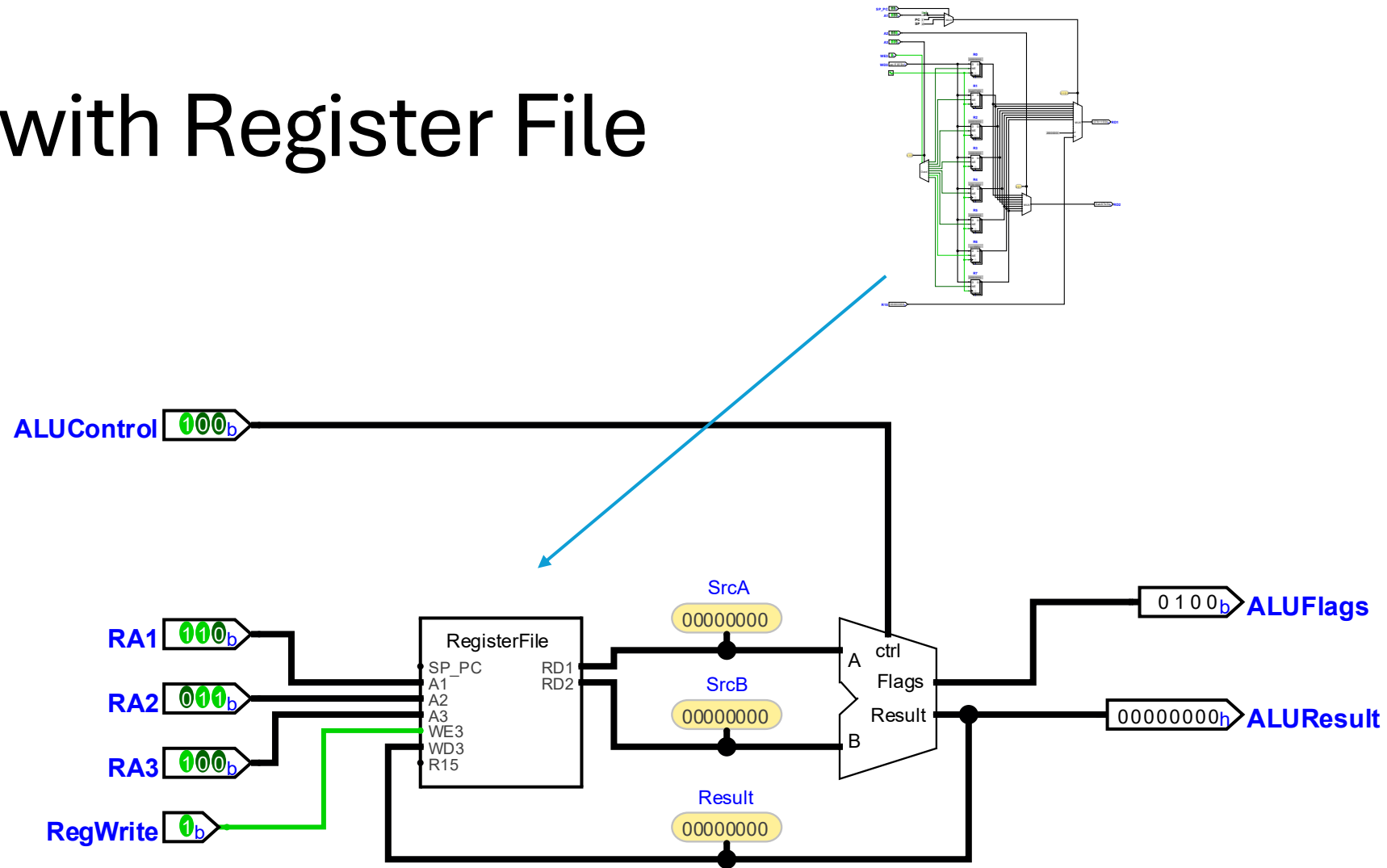




# Instruction Encoding


instruction encoding												assembler					
15			8						0								
0	0	0	0	0	0	0	0	0	0	0	n	n	n	d	d	d	MOV <sub>S</sub> <Rd>,<Rn>
0	0	0	1	1	0	0	0	m	m	m	n	n	n	d	d	d	ADD <sub>S</sub> <Rd>,<Rn>,<Rm>
0	0	0	1	1	0	1	0	m	m	m	n	n	n	d	d	d	SUB <sub>S</sub> <Rd>,<Rn>,<Rm>
0	0	1	0	0	0	0	0	d	d	d	i	i	i	i	i	i	MOV <sub>S</sub> <Rd>, #<imm8>
0	0	1	1	0	0	0	0	dn	dn	dn	i	i	i	i	i	i	ADD <sub>S</sub> <Rdn>,<imm8>
0	0	1	1	1	0	0	0	dn	dn	dn	i	i	i	i	i	i	SUB <sub>S</sub> <Rdn>,<imm8>
1	0	0	1	1	0	0	0	t	t	t	i	i	i	i	i	i	LDR <Rt>,<SP>,<imm8>
1	0	0	1	0	0	0	0	t	t	t	i	i	i	i	i	i	STR <Rt>,<SP>,<imm8>
1	1	0	1	0	0	0	0	c	c	c	c	i	i	i	i	i	Bcc #<sim8>
1	1	1	0	0	0	0	0	i	i	i	i	i	i	i	i	i	B #<sim11>

RegSrc	0 0	use RA1 for A1
	0 1	use PC for A1
	1 0	use SP for A1
0		use individual bits for RAi
1		use bits 10..8 for all RAi

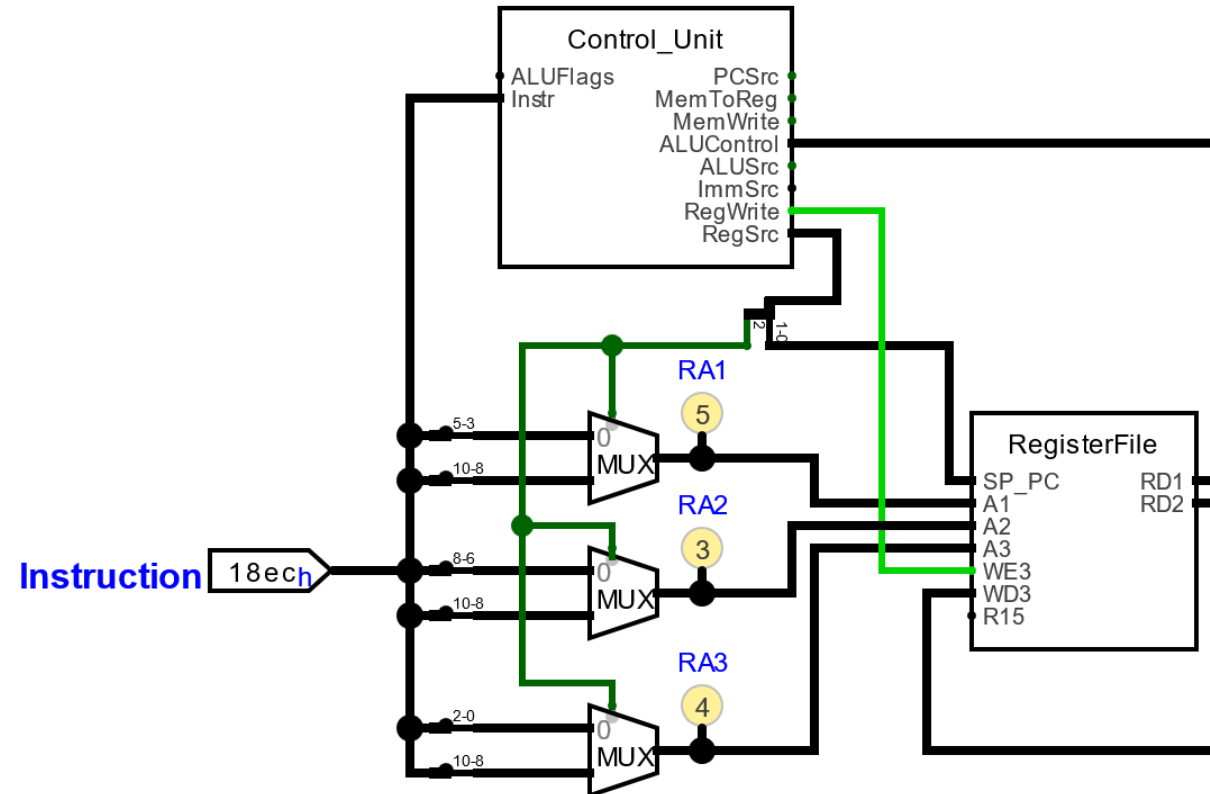

# Instruction Decoder & Control Unit


0	0	0	0	0	0	0	0	0	0	n	n	n	d	d	d	MOVS <Rd>,<Rn>
0	0	0	1	1	0	0	m	m	m	n	n	n	d	d	d	ADDS <Rd>,<Rn>,<Rm>
0	0	0	1	1	0	1	m	m	m	n	n	n	d	d	d	SUBS <Rd>,<Rn>,<Rm>

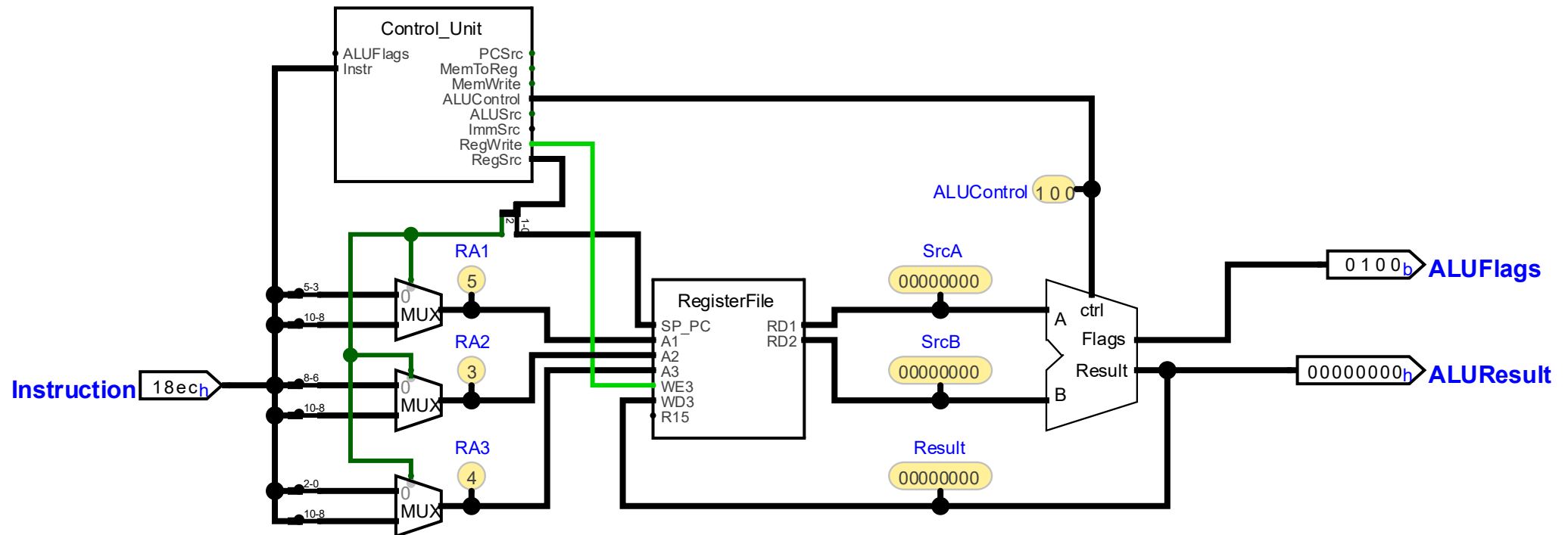

# Immediate Operands

0	0	1	0	0	d	d	d	i	i	i	i	i	i	i	i	MOVS <Rd>, #<imm8>
0	0	1	1	0	dn	dn	dn	i	i	i	i	i	i	i	i	ADDS <Rdn>, #<imm8>
0	0	1	1	1	dn	dn	dn	i	i	i	i	i	i	i	i	SUBS <Rdn>, #<imm8>


ImmSrc	0	0	imm8
	0	1	imm8 << 2
	1	0	simm8 << 1
	1	1	simm11 << 1

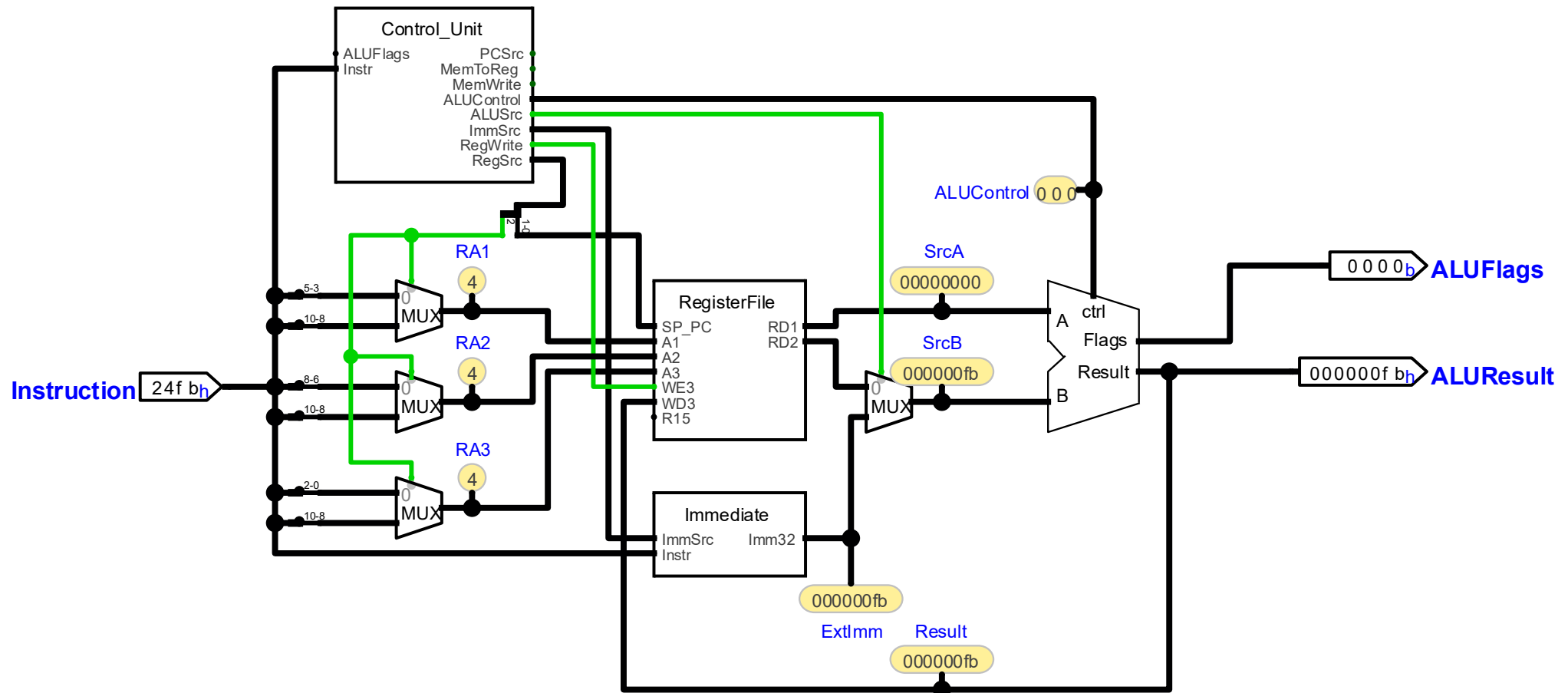

# Instruction Memory


ROM	A	D
	a	ROM[a]

static read

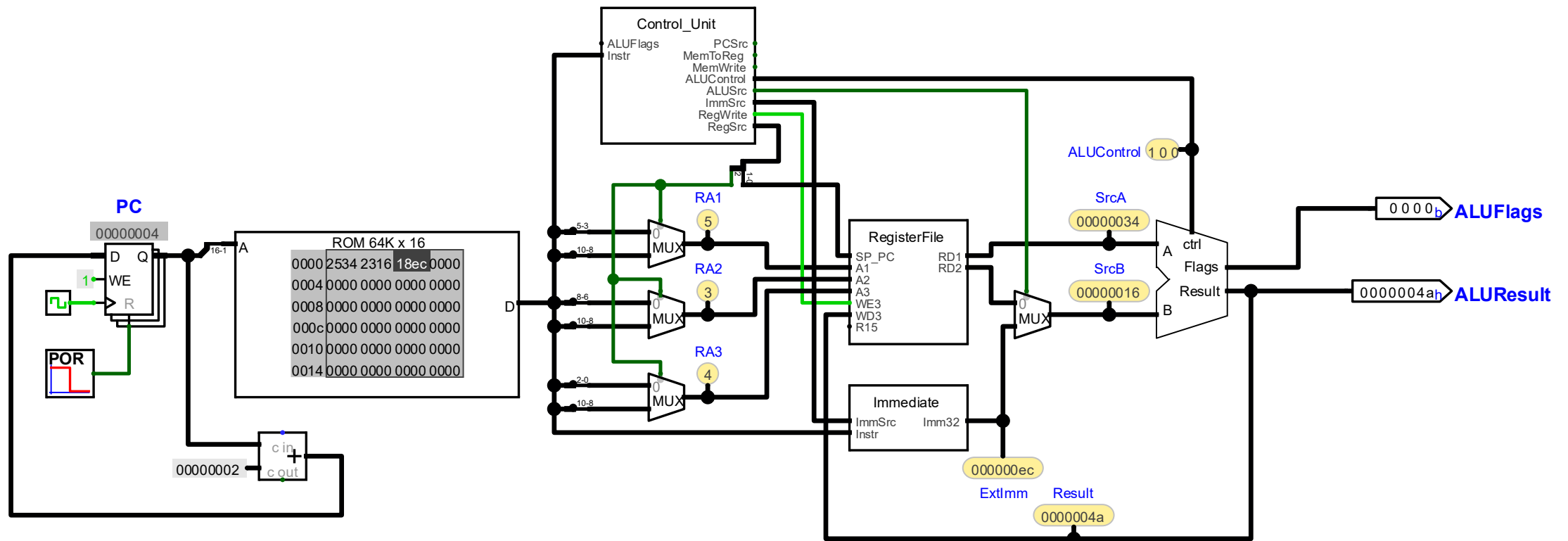

# Branch


1 1 1 0 0 | i i i i i i i i i i

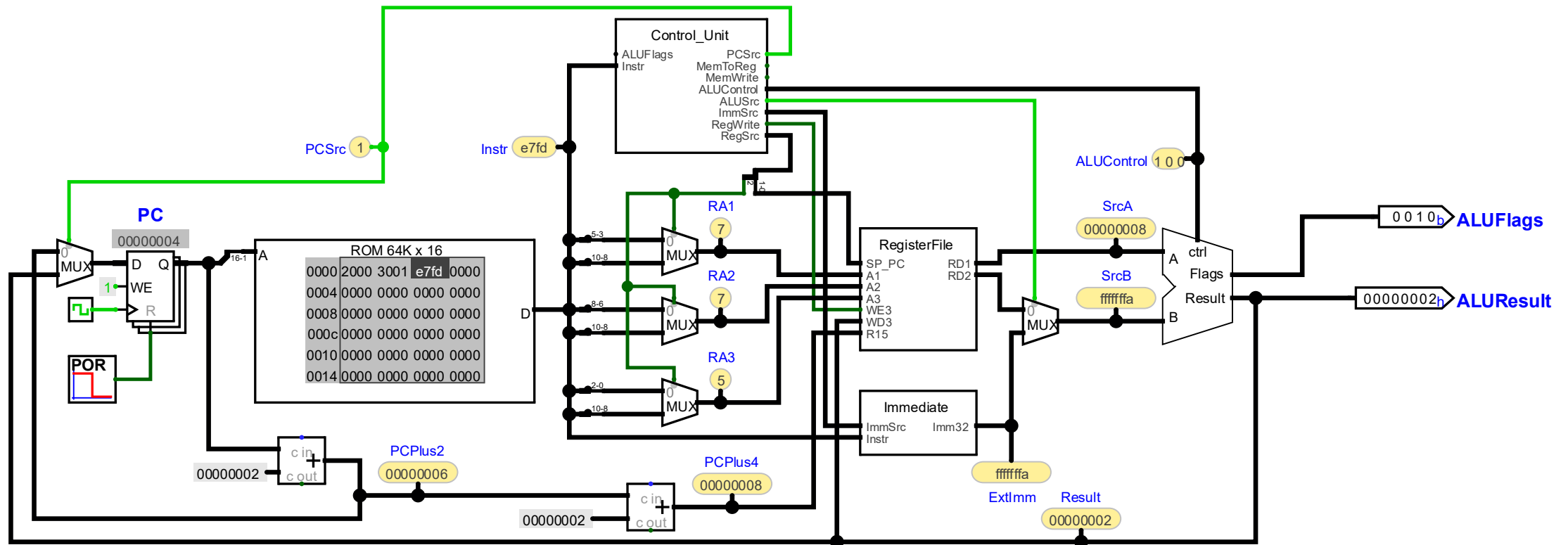

# Conditional Branch

1 1 0 1 | c c c c | i i i i i i i i


Code	Condition	Meaning	Status of Flags
0 0 0 0	EQ	Equal	Z==1
0 0 0 1	NE	Not Equal	Z==0
0 0 1 0	CS or HS	Unsigned Higher or Same (or Carry Set)	C==1
0 0 1 1	CC or L0	Unsigned Lower (or Carry Clear)	C==0
0 1 0 0	MI	Negative (or Minus)	N==1
0 1 0 1	PL	Positive (or Plus)	N==0
0 1 1 0	VS	Signed Overflow	V==1
0 1 1 1	VC	No signed Overflow	V==0
1 0 0 0	HI	Unsigned Higher	(C==1) && (Z!=0)
1 0 0 1	LS	Unsigned Lower or same	(C==0)    (Z==0)
1 0 1 0	GE	Signed Greater Than or Equal	N==V
1 0 1 1	LT	Signed Less Than	N!=V
1 1 0 0	GT	Signed Greater Than	(Z==0) && (N==V)
1 1 0 1	LE	Signed Less Than or Equal	(Z==1)    (N!=V)
1 1 1 0	AL	Always executed	true
1 1 1 1	NV	Never executed	false

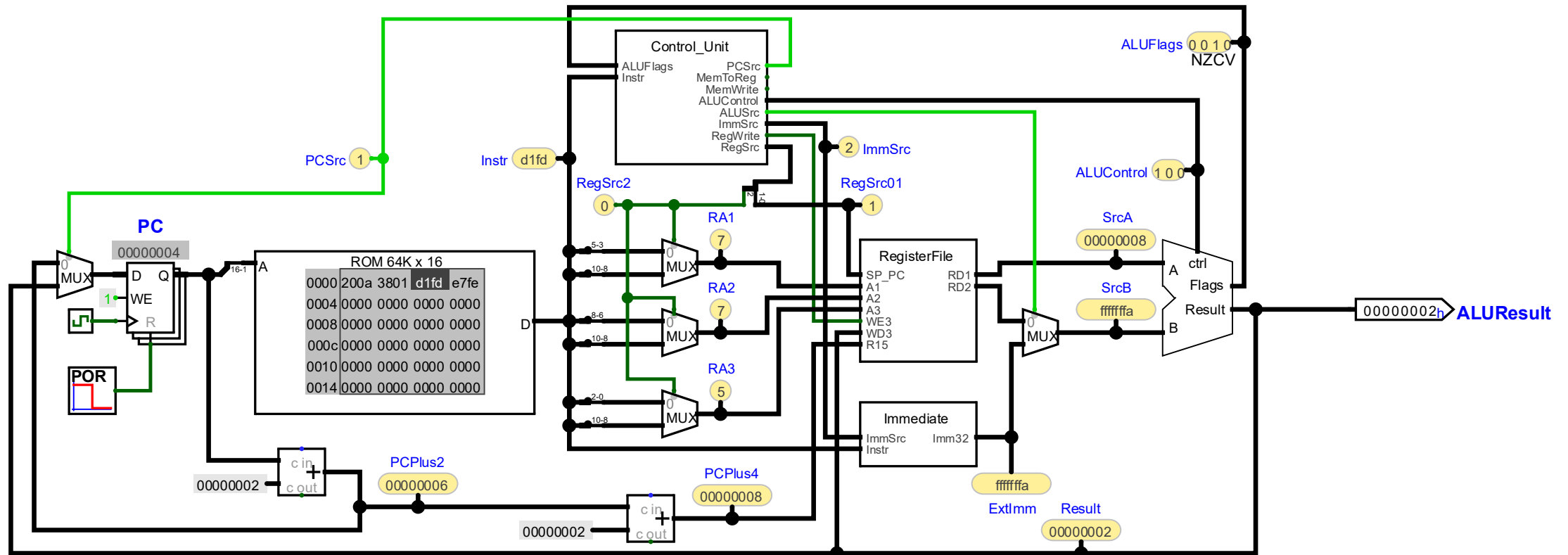

# Store to Data Memory

RAM	C	WE	OE	A	Din	Dout	
x	x	1	a			RAM[a]	static read
↑	1	x	a	RAM[a] = Din			rising edge triggered write


1 0 0 1 0 | t t t | i i i i i i i i

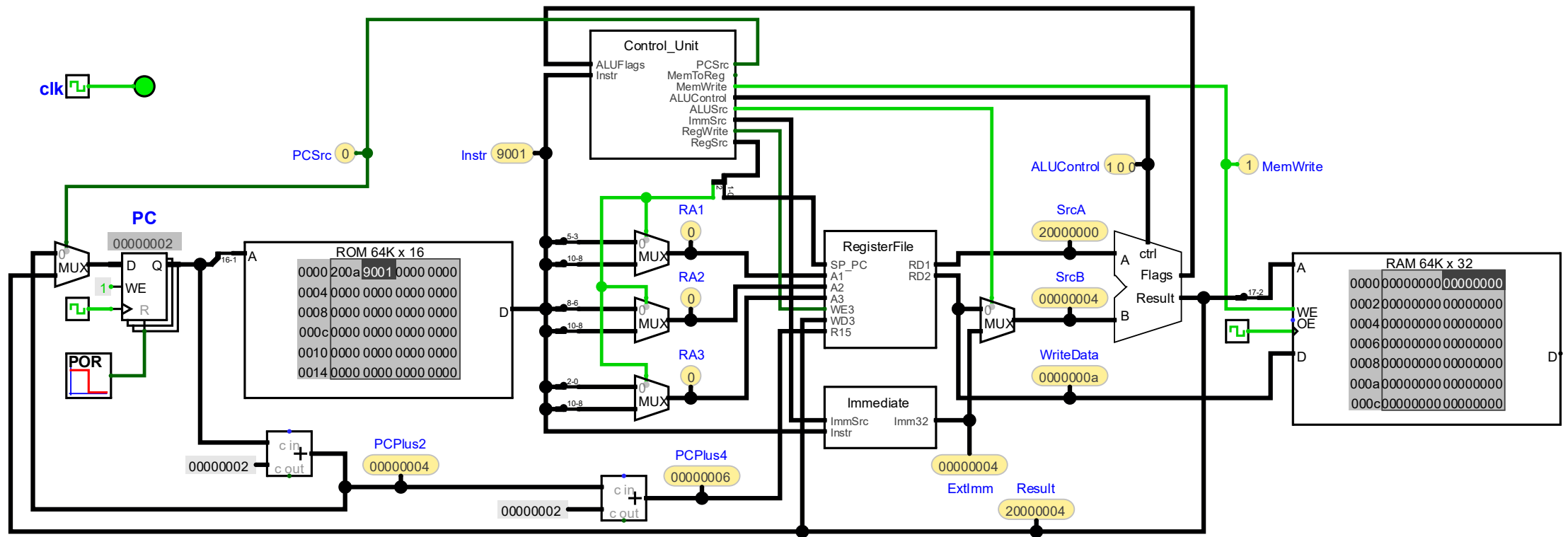

# Load from Data Memory

RAM	C	WE	OE	A	Din	Dout	
	x	x	1	a		RAM[a]	static read
	↑	1	x	a	RAM[a] = Din		rising edge triggered write

1 0 0 1 1 | t t t | i i i i i i i i

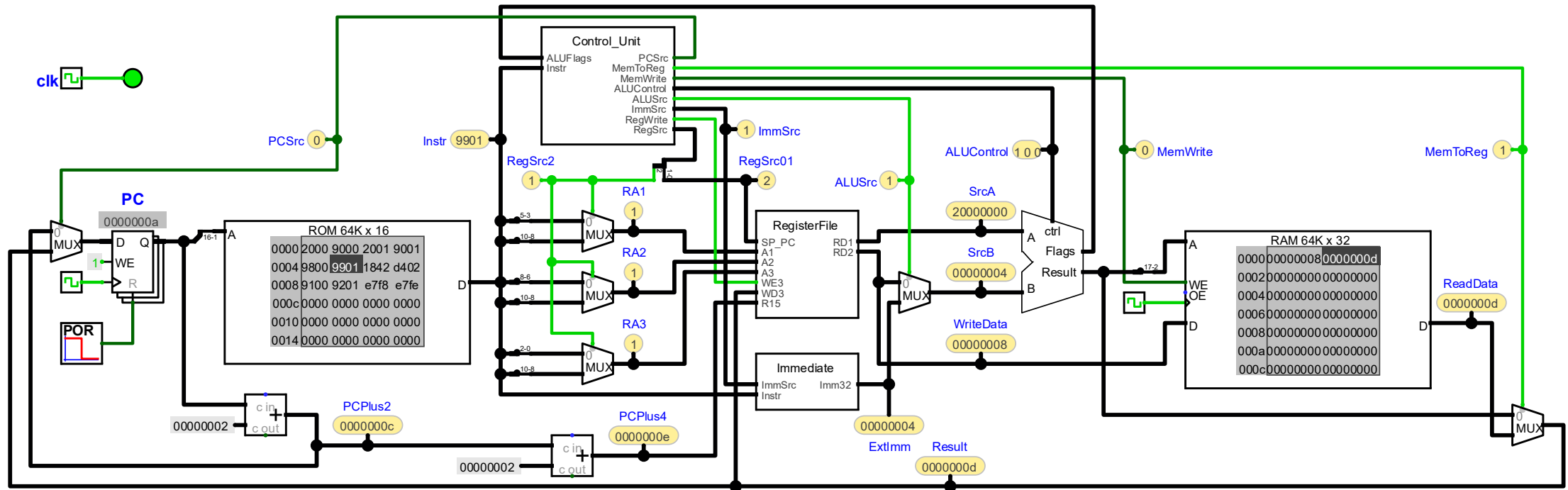




# Instructions

# MOVS <Rd>, #<imm8>

```
00 10 0 Rd. ....imm8
```

ImmSrc	0	0	imm8	ALUControl	0	0	0	B
	0	1	imm8 << 2		0	0	1	-B
	1	0	simm8 << 1		0	1	0	0
	1	1	simm11 << 1		0	1	1	A
					1	0	0	A+B
					1	0	1	A-B
					1	1	0	A&B
					1	1	1	A B

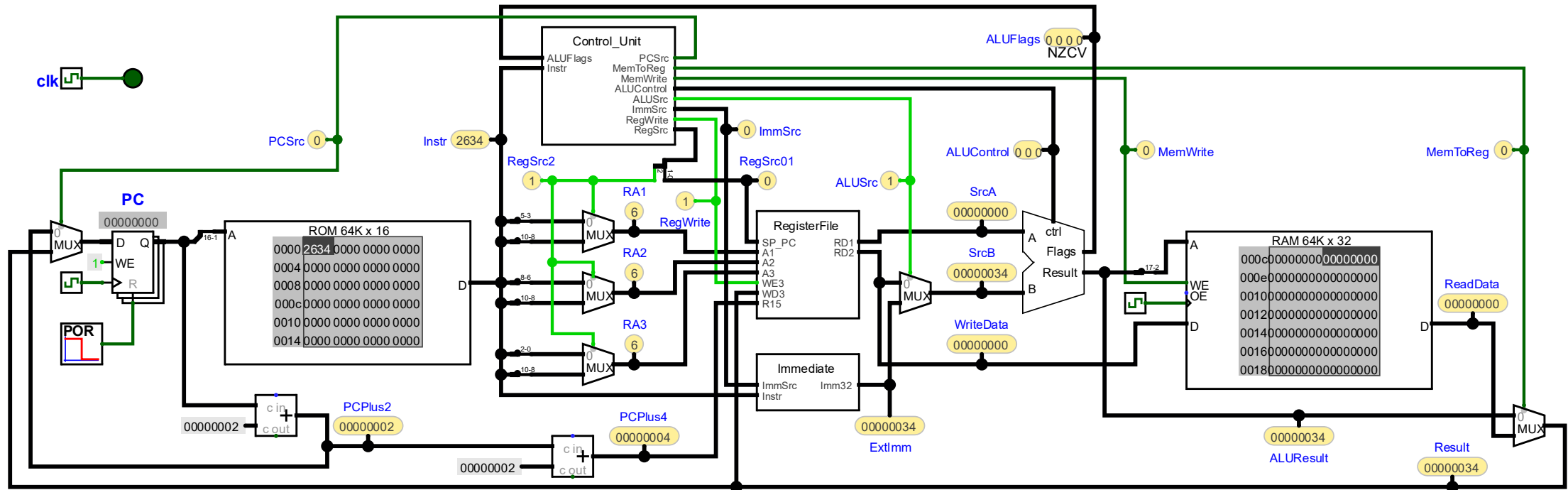


# ADDS <Rdn>, #<imm8>

0011 0 Rdn ....imm8

ImmSrc	0	0	imm8
	0	1	imm8 << 2
	1	0	simm8 << 1
	1	1	simm11 << 1

ALUControl	0	0	0	B
	0	0	1	-B
	0	1	0	0
	0	1	1	A
	1	0	0	A+B
	1	0	1	A-B
	1	1	0	A&B
	1	1	1	A B

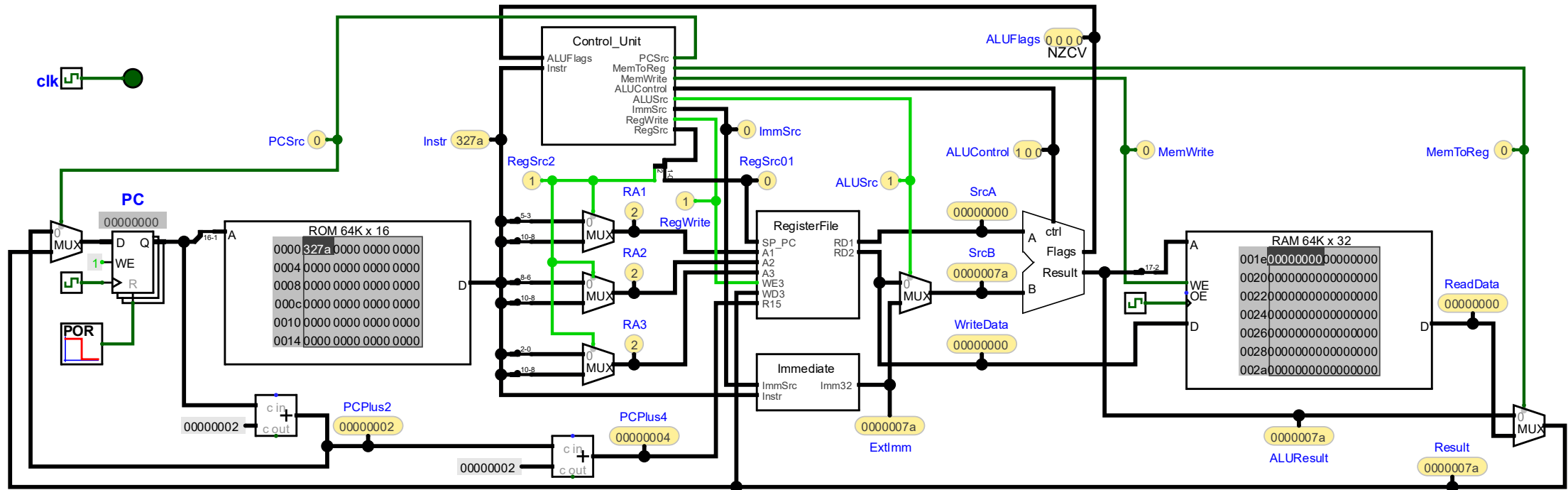


# SUBS <Rdn>, #<imm8>

00 11 1 Rdn ....imm8

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

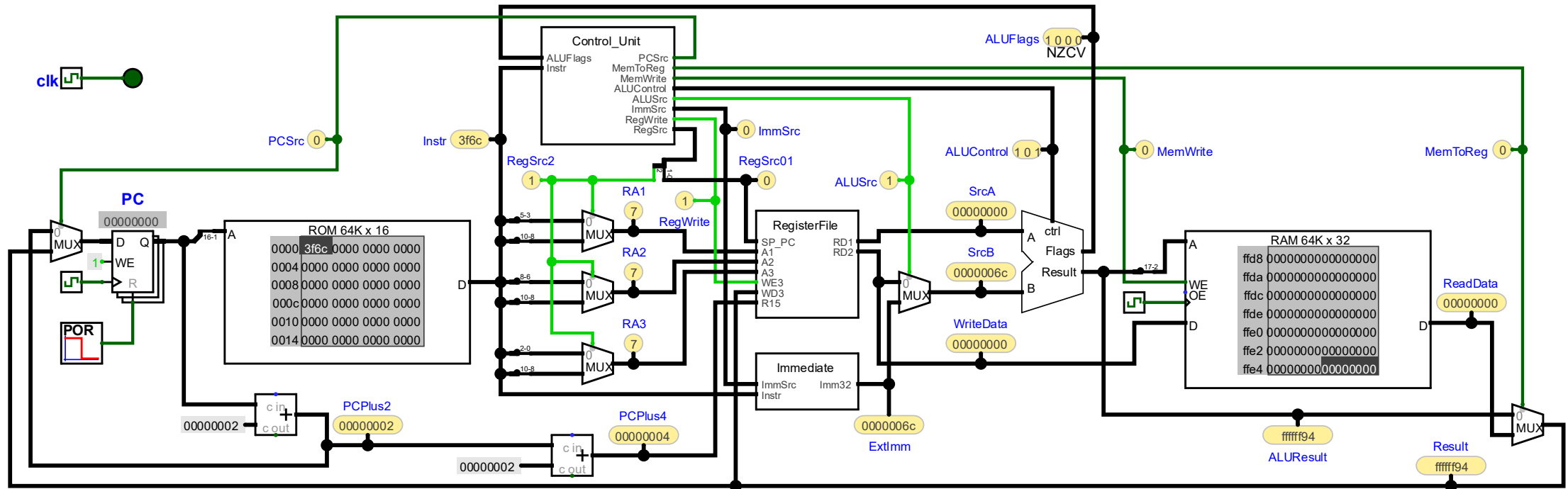


# MOVS <Rd>,<Rm>

00 00 0 00000 Rm. Rd.

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

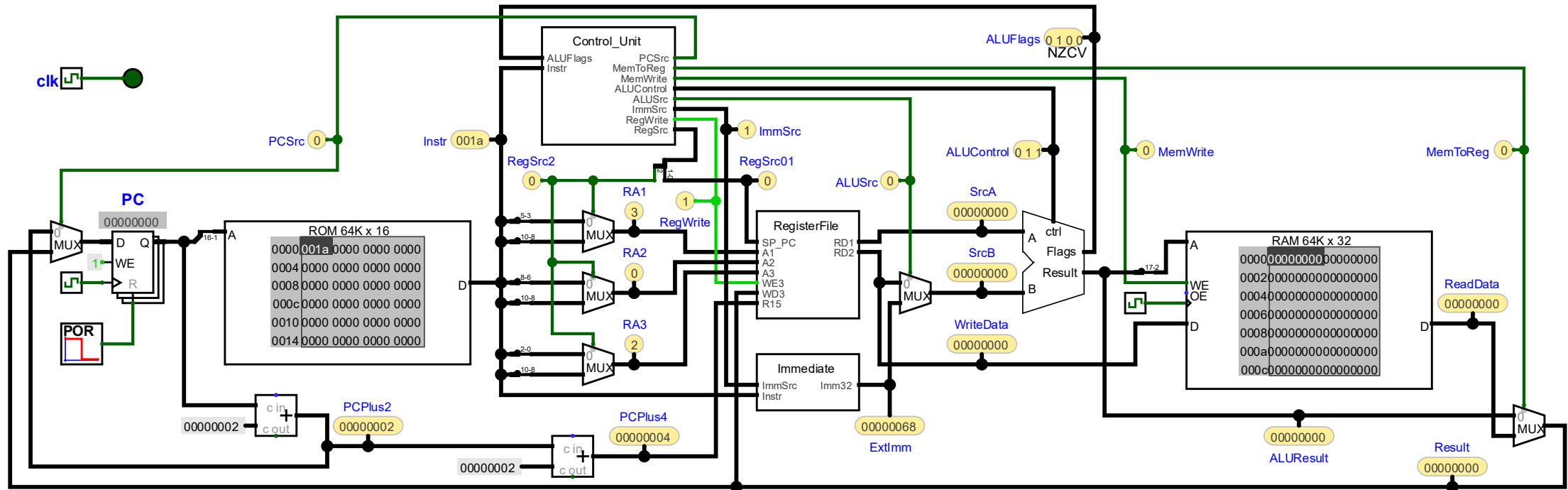


# ADDS <Rd>,<Rn>,<Rm>

00 01 1 00 Rm. Rn. Rd.

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

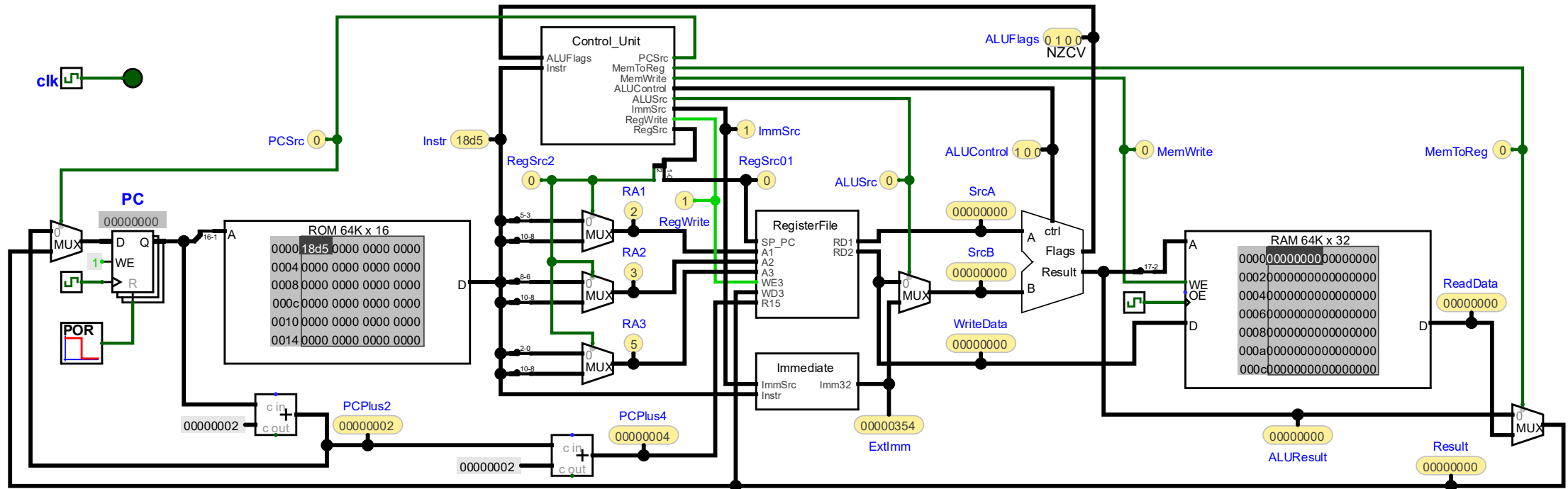


# SUBS <Rd>,<Rn>,<Rm>

00 01 1 01 Rm. Rn. Rd.

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

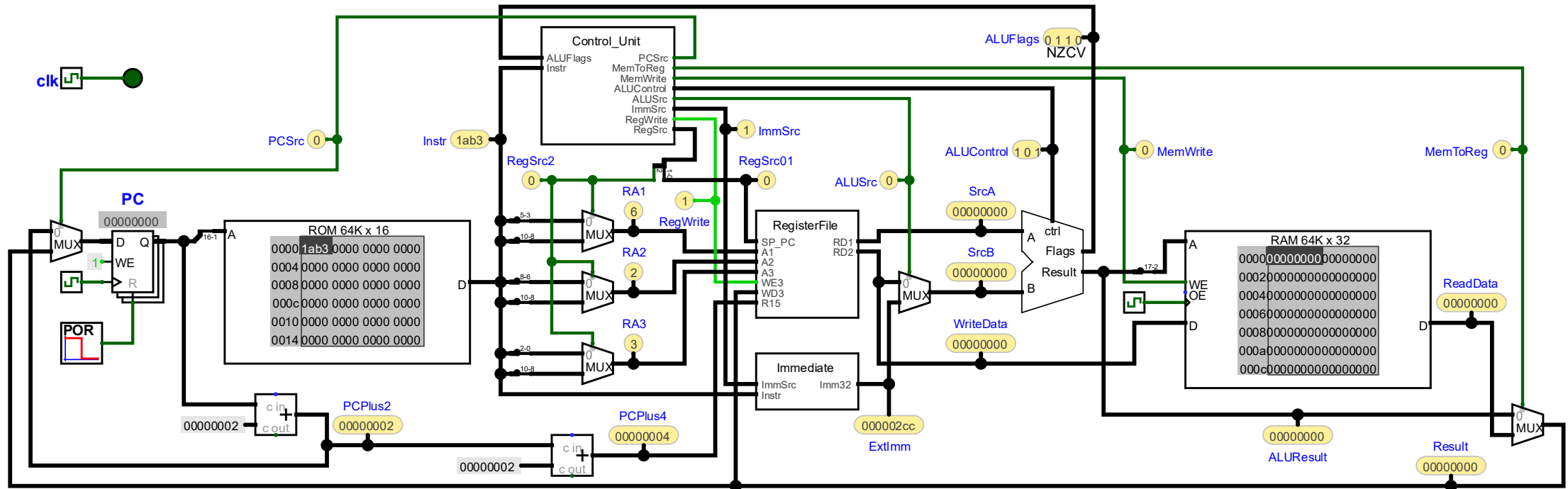


# LDR <Rt>, [SP, #<imm8>]

10 01 1 Rt. ....imm8

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

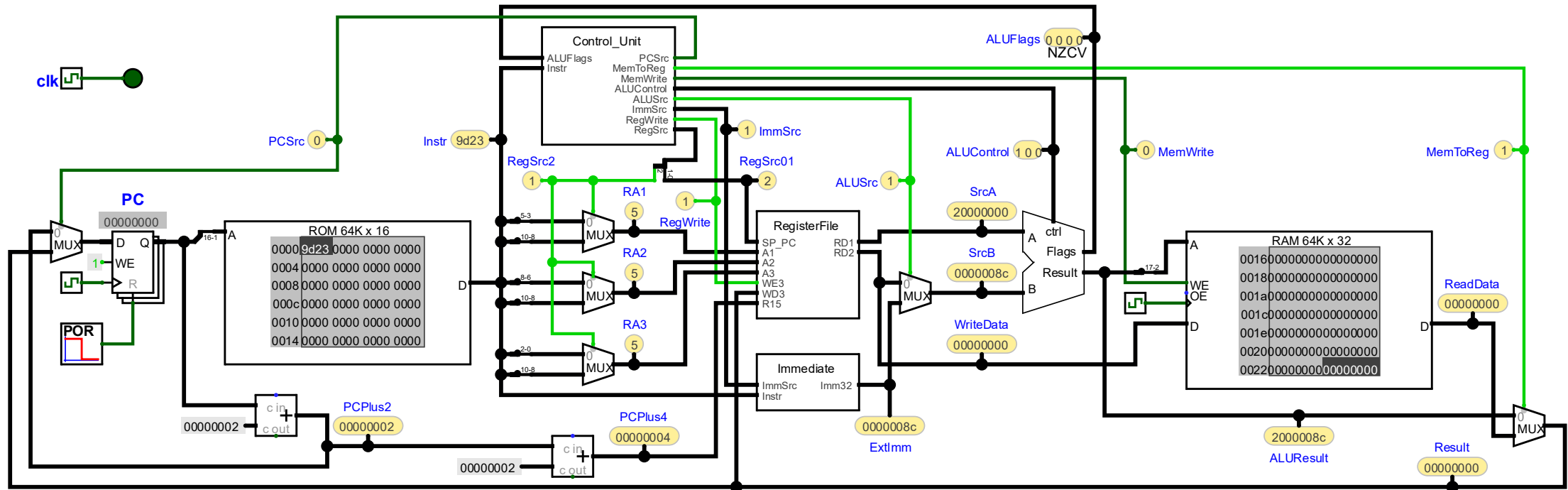




# STR <Rt>, [SP, #<imm8>]

10 01 0 Rt. ....imm8

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

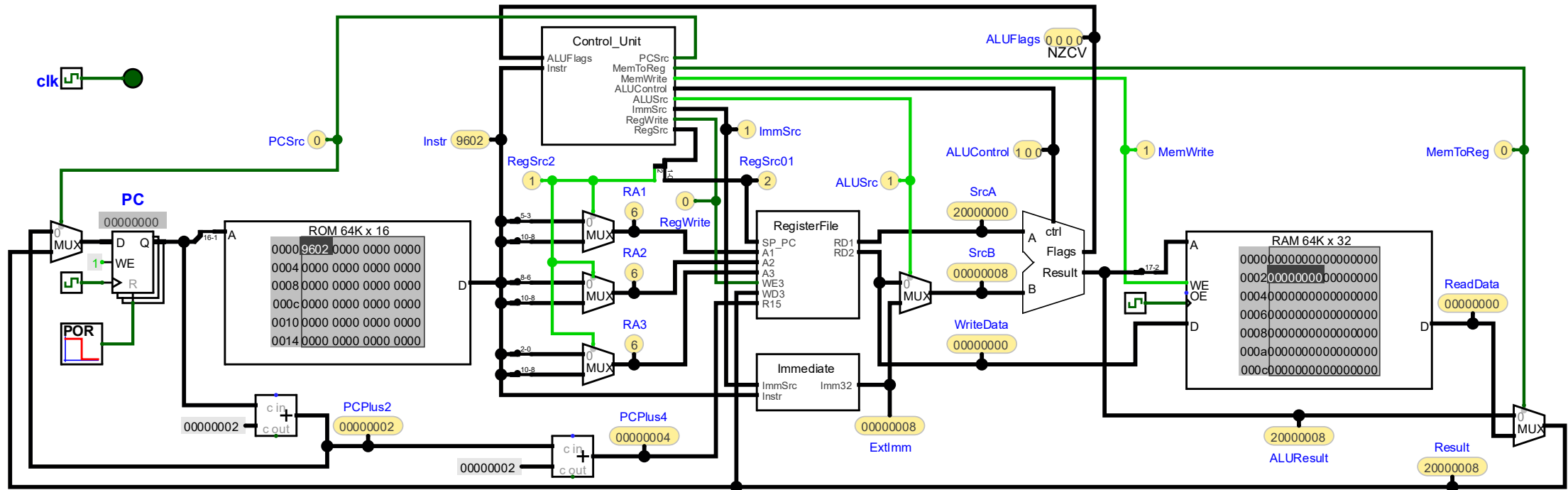


# Bcc #<sim8>

11 01 cond ...simm8

ImmSrc 0 0 imm8  
 0 1 imm8 << 2  
 1 0 simm8 << 1  
 1 1 simm11 << 1

ALUControl 0 0 0 B  
 0 0 1 -B  
 0 1 0 0  
 0 1 1 A  
 1 0 0 A+B  
 1 0 1 A-B  
 1 1 0 A&B  
 1 1 1 A|B

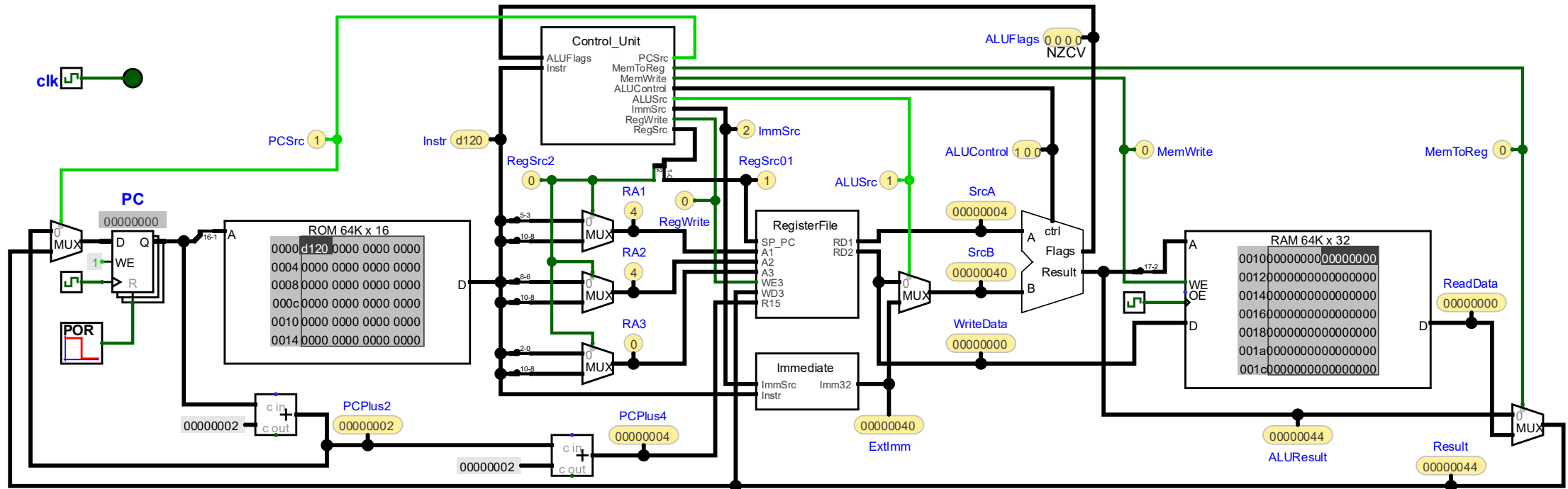


# B #<simm11>

11 10 0 .....simm11

ImmSrc	0	0	imm8
	0	1	imm8 << 2
	1	0	simm8 << 1
	1	1	simm11 << 1

ALUControl	0	0	0	B
	0	0	1	-B
	0	1	0	0
	0	1	1	A
	1	0	0	A+B
	1	0	1	A-B
	1	1	0	A&B
	1	1	1	A B

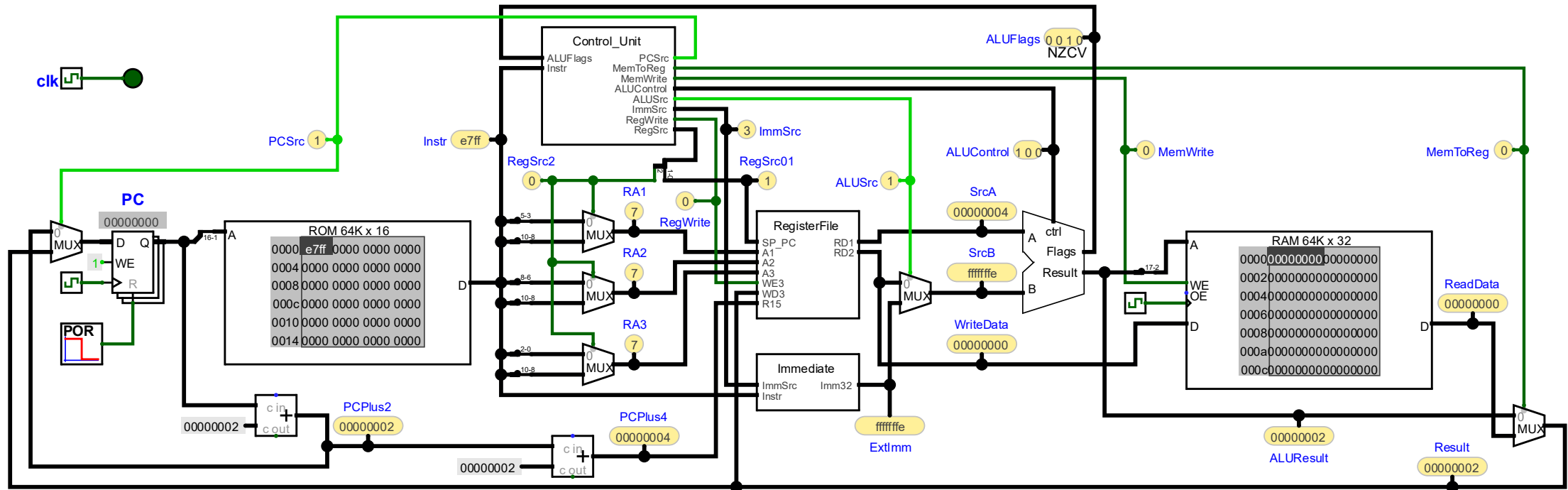

# Timing Diagrams

